


Arithmetic / Logic Unit – ALU Design

Presentation F

Slides by Gojko Babić

07/19/2005

32-bit ALU

 

- Our ALU should be able to perform functions:
 - logical **and** function
 - logical **or** function
 - arithmetic **add** function
 - arithmetic **subtract** function
 - arithmetic **slt (set-less-then)** function
 - logical **nor** function
- ALU control lines define a function to be performed on A and B.


g. babic

Presentation F

2

Functioning of 32-bit ALU

Function	ALU Control lines		
	Ainvert	Binvert	Operation
and	0	0	00
or	0	0	01
add	0	0	10
subtract	0	1	10
slt	0	1	11
nor	1	1	00

 

- **Result** lines provide result of the chosen function applied to values of A and B
- Since this ALU operates on 32-bit operands, it is called **32-bit ALU**
- **Zero** output indicates if all Result lines have value 0
- **Overflow** indicates a sign integer overflow of add and subtract functions; for unsigned integers, this overflow indicator does not provide any useful information
- **Carry out** indicates carry out and **unsigned integer overflow**


g. babic

Presentation F

3

Designing 32-bit ALU: Beginning

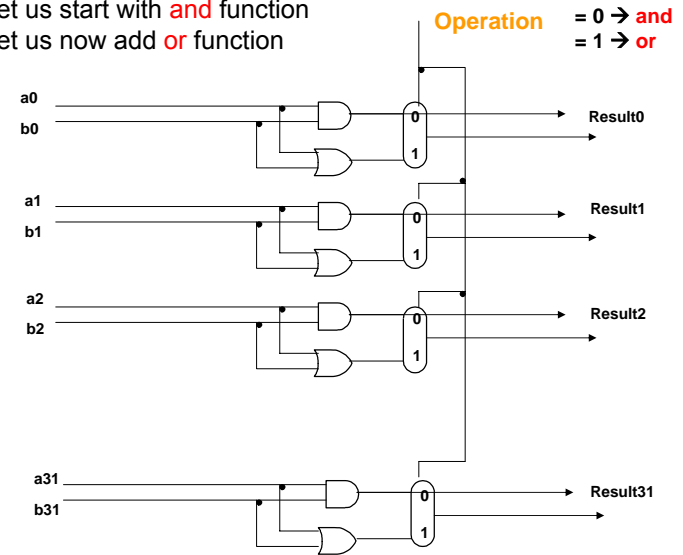1. Let us start with **and** function
2. Let us now add **or** function




g. babic

4

Designing 32-bit ALU: Principles


- Number of functions are performed internally, but only one result is chosen for the output of ALU

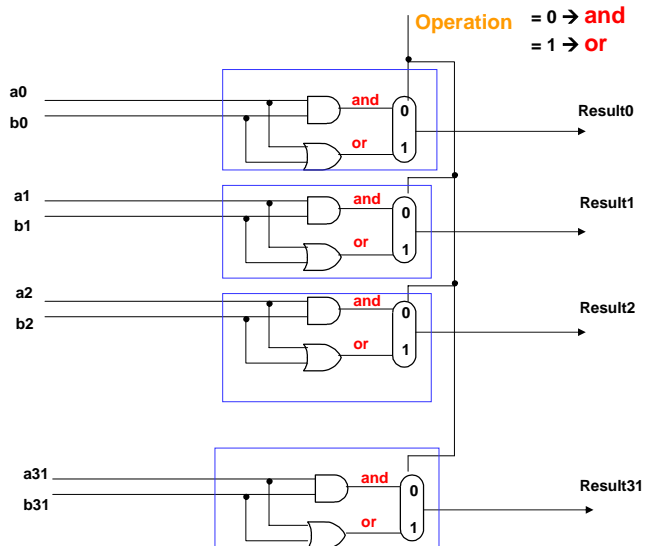- 32-bit ALU is built out of 32 identical 1-bit ALU's



Designing Adder

 
- 32-bit adder is built out of 32 1-bit adders




1-bit Adder Truth Table

Input			Output	
a	b	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 From the truth table and after minimization, we can have this design for CarryOut




32-bit Adder

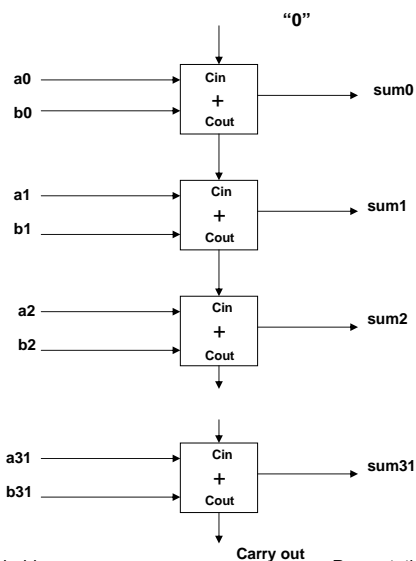


This is a ripple carry adder.

The key to speeding up addition is determining carry out in the higher order bits sooner.
Result: Carry look-ahead adder.

32-bit ALU With 3 Functions

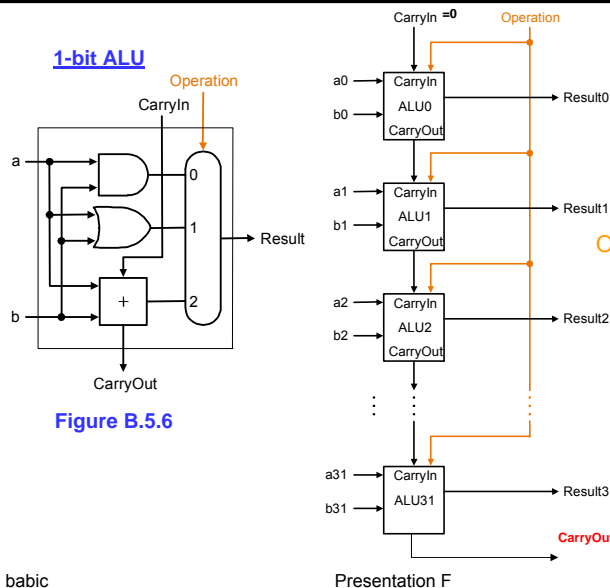

32-bit Subtractor

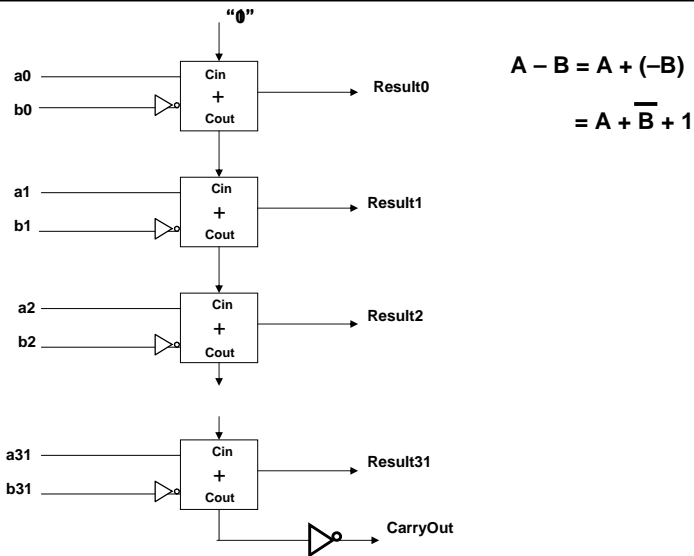


g. babic

Presentation F

9


32-bit Adder / Subtractor

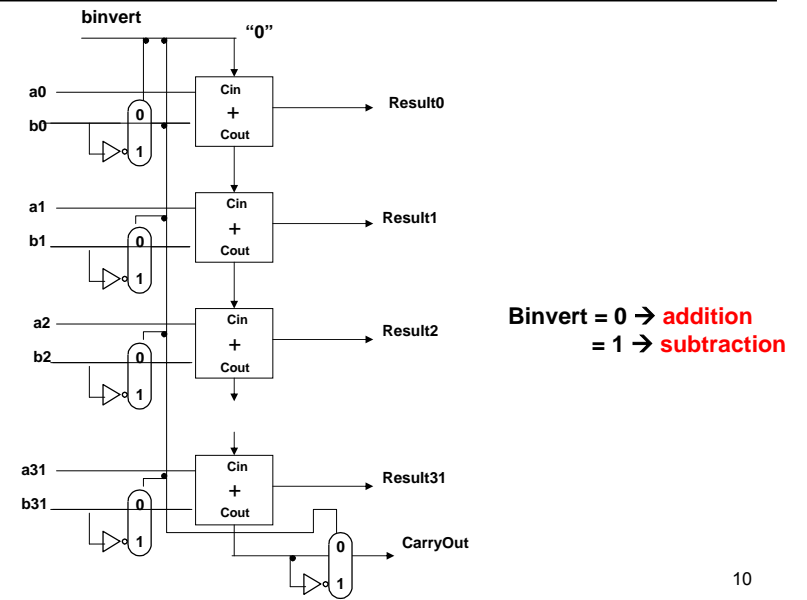

g. babic

10

32-bit ALU With 4 Functions

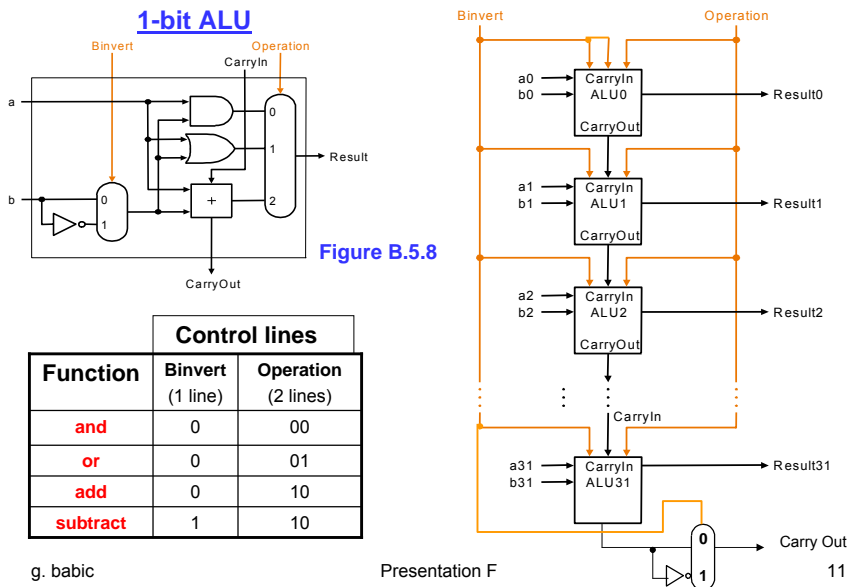


g. babic

Presentation F

11

2's Complement Overflow

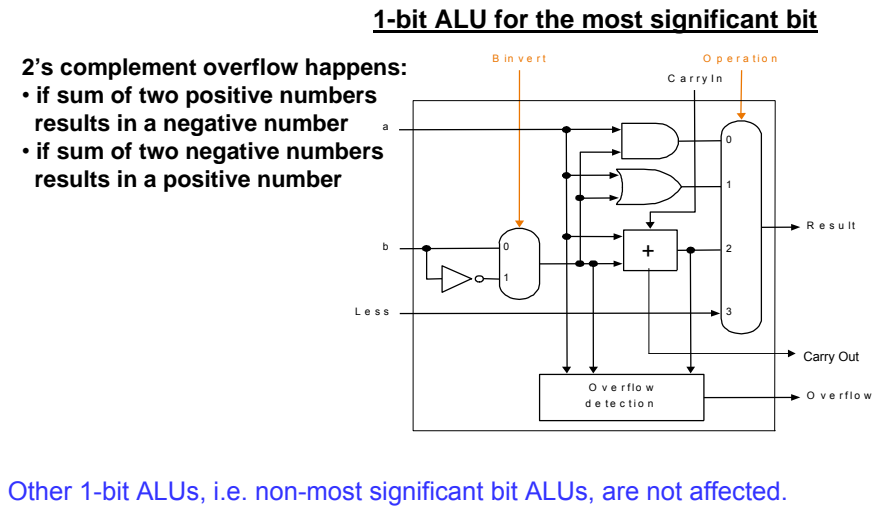

Other 1-bit ALUs, i.e. non-most significant bit ALUs, are not affected.


g. babic

Presentation F

12

32-bit ALU With 4 Functions and Overflow

Function	Control lines	
	Binvert (1 line)	Operation (2 lines)
and	0	00
or	0	01
add	0	10
subtract	1	10

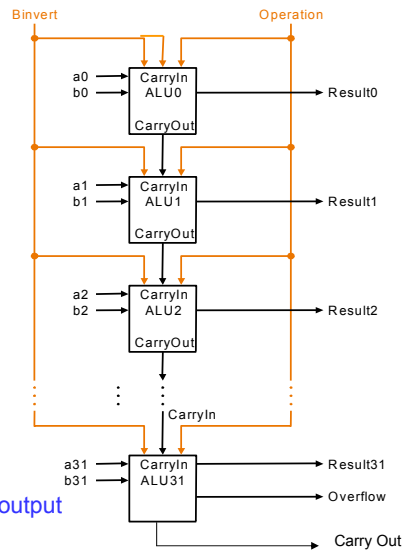

Missing: **slt** & **nor** functions and **Zero** output

g. babic

Presentation F

Add correction for CarryOut

Set Less Than (slt) Function

- **slt** function is defined as:

$$A \text{ slt } B = \begin{cases} 000 \dots 001 & \text{if } A < B, \text{ i.e. if } A - B < 0 \\ 000 \dots 000 & \text{if } A \geq B, \text{ i.e. if } A - B \geq 0 \end{cases}$$

- Thus each 1-bit ALU should have an additional input (called "Less"), that will provide results for **slt** function. This input has value 0 for all but 1-bit ALU for the least significant bit.
- For the least significant bit **Less** value should be sign of $A - B$


g. babic

Presentation F


14

32-bit ALU With 5 Functions

1-bit ALU for non-most significant bits

 


1-bit ALU for the most significant bits

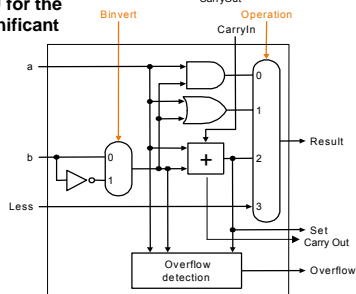


Operation = 3 and Binvert = 1 for **slt** function

Add correction for CarryOut

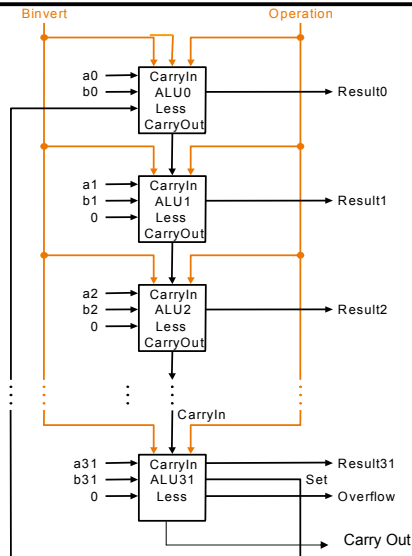

32-bit ALU with 5 Functions and Zero

Function	Control lines	
	Binvert (1 line)	Operation (2 lines)
and	0	00
or	0	01
add	0	10
subtract	1	10
slt	1	11

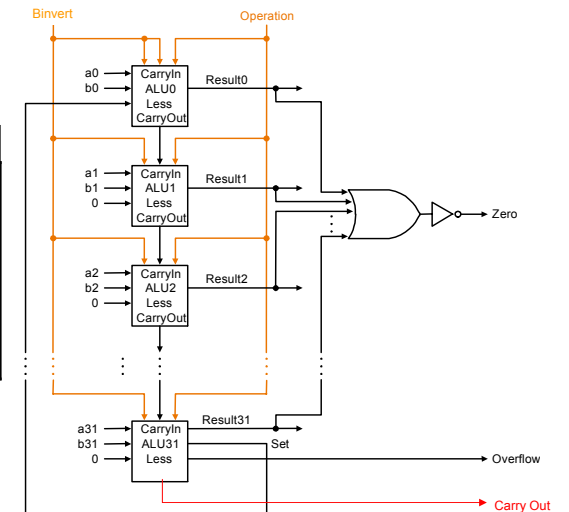

g. babic

Presentation F

Add correction for CarryOut

32-bit ALU with 6 Functions

$$A \text{ nor } B = \overline{A} \text{ and } \overline{B}$$

 


Figure B.5.10 (Top)

Function	Ainvert	Binvert	Operation
and	0	0	00
or	0	0	01
add	0	0	10
subtract	0	1	10
slt	0	1	11
nor	1	1	00

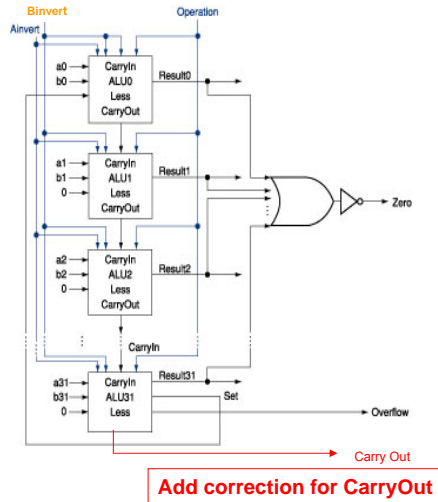


Figure B.5.12
+ Carry Out + Binvert

17

32-bit ALU Elaboration

- We have now accounted for all but one of the arithmetic and logic functions for the core MIPS instruction set. 32-bit ALU with 6 functions omits support for shift instructions.
- It would be possible to widen 1-bit ALU multiplexer to include 1-bit shift left and/or 1-bit shift right.
- Hardware designers created the circuit called a barrel shifter, which can shift from 1 to 31 bits in no more time than it takes to add two 32-bit numbers. Thus, shifting is normally done outside the ALU.
- We now consider integer multiplication (but not division).

g. babic

Presentation F

18

Multiplication

- Multiplication is more complicated than addition:
 - accomplished via shifting and addition
- More time and more area required
- Let's look at 3 versions based on elementary school algorithm
- Example of **unsigned** multiplication:

$$\begin{array}{r}
 \text{5-bit multiplicand} \quad 10001_2 = 17_{10} \\
 \text{5-bit multiplier} \quad \times 10011_2 = 19_{10} \\
 \hline
 10001 \\
 10001 \\
 00000 \\
 00000 \\
 10001 \\
 \hline
 101000011_2 = 323_{10}
 \end{array}$$
- But, this algorithm is very impractical to implement in hardware

g. babic

Presentation F

19

Multiplication : Example

- The multiplication can be done with intermediate additions.
- The same example:

multiplicand	10001
multiplier	$\times 10011$
intermediate product	000000000
add since multiplier bit=1	<u>10001</u>
intermediate product	0000010001
shift multiplicand and add since multiplier bit=1	<u>10001</u>
intermediate product	0000110011
shift multiplicand and no addition since multiplier bit=0	
shift multiplicand and no addition since multiplier bit=0	
shift multiplicand and add multiplier since bit=1	<u>10001</u>
final result	0101000011

g. babic

Presentation F

20

Multiplication Hardware: 1st Version

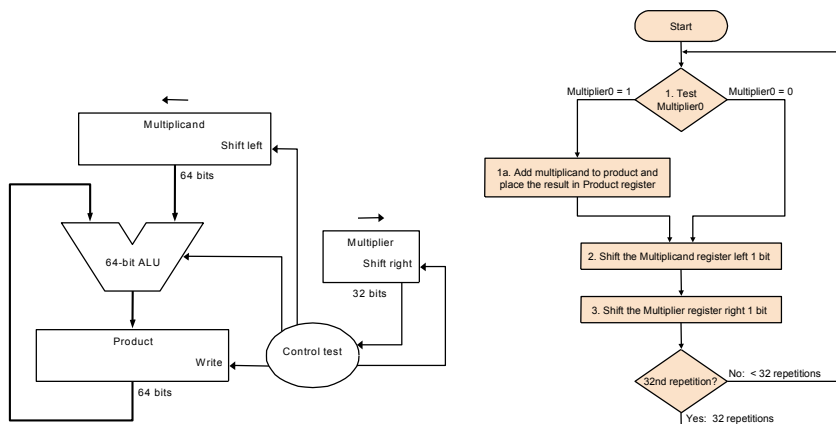


Figure 3.5

g. babic

Presentation F

21


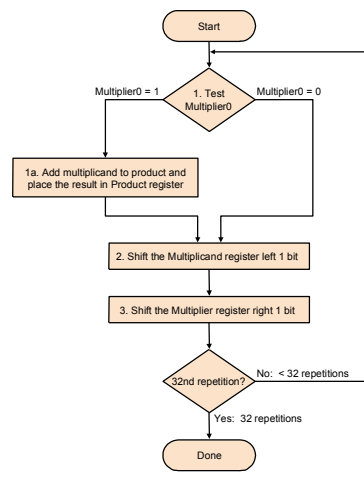


Figure 3.6


Multiplication Hardware: 2nd Version

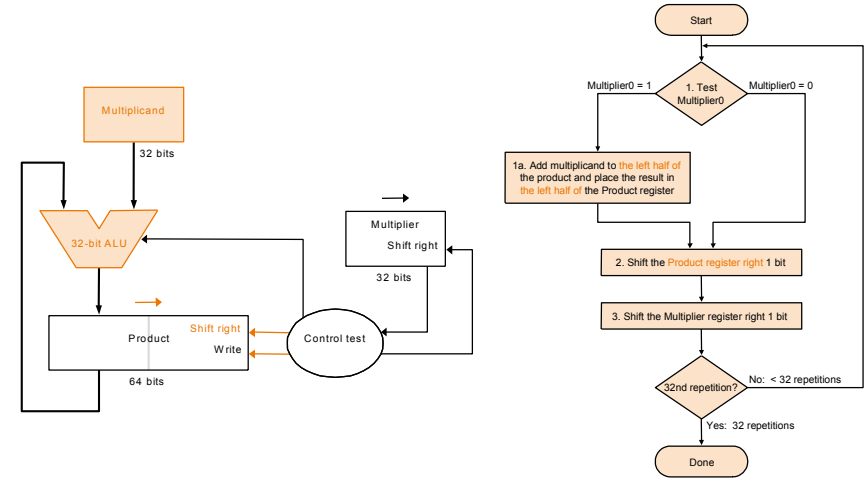

g. babic

Presentation F

22

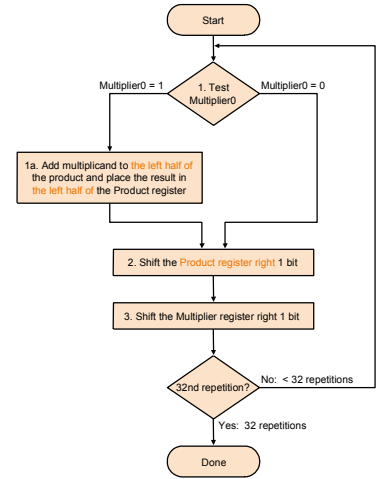

Multiplication Hardware: 3rd Version


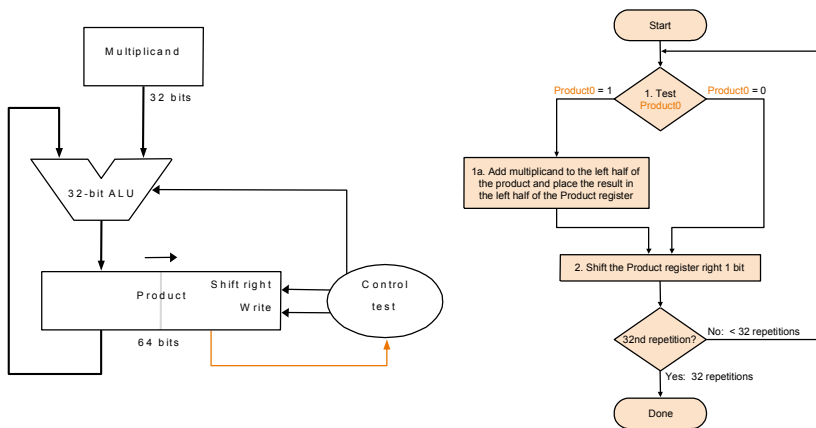


Figure 3.7

g. babic

Presentation F

23

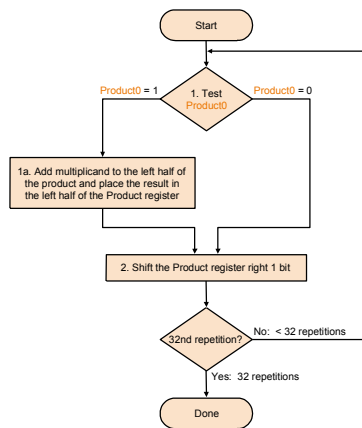

Multiplication of Signed Integers

- A simple algorithm:
 - Convert to positive integer any of operands (if needed) and remember original signs
 - Perform multiplication of unsigned numbers using the existing algorithm and hardware
 - Negate product if original signs disagree
- This algorithm is not simple to implement in hardware, since it has to:
 - account in advance about signs,
 - if needed, convert from negative to positive numbers,
 - if needed, convert back to negative integer at the end
- **Fast multiplication algorithms.**

g. babic

Presentation F

24

Real Numbers

• **Conversion from real binary to real decimal**

– $1101.1011_2 = -13.6875_{10}$

since: $1101_2 = 2^3 + 2^2 + 2^0 = 13_{10}$ and

$0.1011_2 = 2^{-1} + 2^{-3} + 2^{-4} = 0.5 + 0.125 + 0.0625 = 0.6875_{10}$

• **Conversion from real decimal to real binary:**

$+927.45_{10} = +1110011111.011100110011001100 \dots$

$927/2 = 463 + \frac{1}{2} \leftarrow \text{LSB}$ $0.45 \times 2 = 0.9$

$463/2 = 231 + \frac{1}{2}$ $0.9 \times 2 = 1.8$

$231/2 = 115 + \frac{1}{2}$ $0.8 \times 2 = 1.6$

$155/2 = 77 + \frac{1}{2}$ $0.6 \times 2 = 1.2$

$57/2 = 28 + \frac{1}{2}$ $0.2 \times 2 = 0.4$

$28/2 = 14 + 0$ $0.4 \times 2 = 0.8$

$14/2 = 7 + 0$ $0.8 \times 2 = 1.6$


$7/2 = 3 + \frac{1}{2}$ $0.6 \times 2 = 1.2$

$3/2 = 1 + \frac{1}{2}$ $0.2 \times 2 = 0.4$


$1/2 = 0 + \frac{1}{2}$ $0.4 \times 2 = 0.8 \dots$

Floating Point Number Formats

 - The term floating point number refers to representation of real binary numbers in computers.
- IEEE 754 standard defines standards for floating point representations
- Single precision:



- Double precision:

 

Converting to Floating Point

1. Normalize binary real number i.e. put it into the normalized form:

$(-1)^s \times 1.\text{Fraction} \times 2^{\text{Exp}}$

$-1101.1011_2 = (-1)^1 \times 1.1011011 \times 2^3$

$+1110011111.011100 = (-1)^0 \times 1.11001111011100 \times 2^9$

2. Load fields of single or double precision format with values from normalized form, but with the adjustment for E field.

$E = \text{Exp} + 127_{10} = \text{Exp} + 01111111_2$ for single precision

$E = \text{Exp} + 1023_{10} = \text{Exp} + 0111111111_2$ for double precision

- E is called a biased exponent.

Floating Point: Example 1

- Find single and double precision of -13.6875_{10}
Normalized form: $(-1)^1 \times 1.1011011 \times 2^3$

– single precision:

$E = 11_2 + 01111111_2 = 10000010_2$

$1|10000010|101101100000000000000000$

– double precision

$E = 11_2 + 0111111111_2 = 10000000010_2$

$1|10000000010|101101100000000000000000$

00

Floating Point: Example 2

- Find single and double precision of $+927.45_{10}$
 Normalized form: $(-1)^0 \times 1.110011111011\overline{1100} \times 2^9$
 - single precision
 $E = 1001_2 + 01111111_2 = 10001000_2$
 $\underline{0|10001000|11001111101110011001100|1100\dots}$
 truncation $\underline{0|10001000|11001111101110011001100|}$
 rounding $\underline{0|10001000|11001111101110011001101|}$
 - double precision
 $E = 1001_2 + 01111111111_2 = 10000001000$
 $\underline{0|10000001000|11001111101110011001|}$
 $\underline{11001100110011001100110011001|11001100\dots}$
- truncation $\underline{11001100110011001100110011001|}$
 rounding $\underline{11001100110011001100110011010|}$

Converting to Floating Point: Conclusion

- Rules for biased exponents in single precision apply only for real exponents in the range $[-126, 127]$, thus we can have biased exponents only in the range $[1, 254]$.
- The number 0.0 is represented as $S=0, E=0$ and Fraction=0. The infinite number is represented with $E=255$. There are some additional rules that are outside our scope.
- Find the largest (non-infinite) real binary number (by magnitude) which can be represented in a single precision.
 - Floating point overflow
- Find the smallest (non-zero) real binary number (by magnitude) which can be represented in a single precision.
 - Floating point underflow

Floating Point Addition

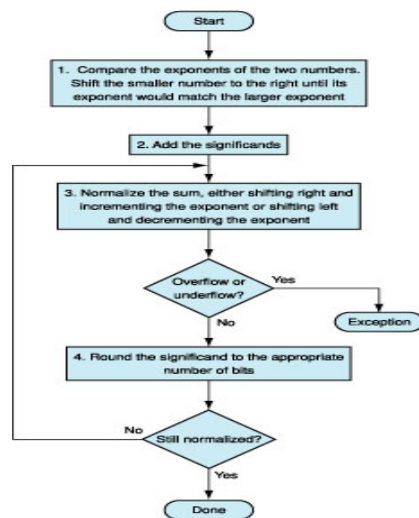


Figure 3.16

Arithmetic Unit for Floating Point Addition


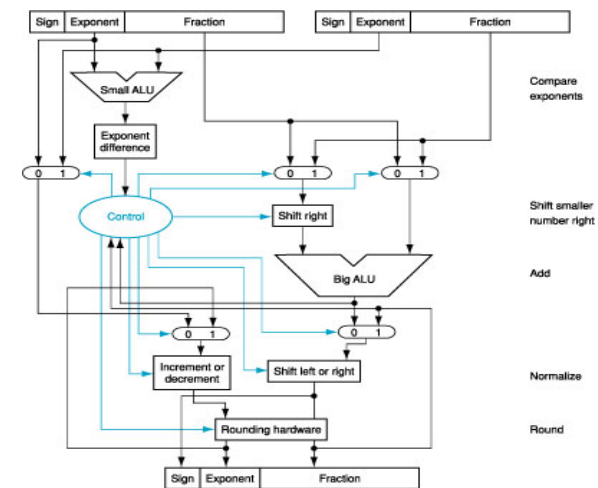
 


Figure 3.17

32-bit ALU with 6 Functions

 

g. babic