


Arithmetic / Logic Unit – ALU Design

Presentation F

Reading Assignment: B5, 3.4

Slides by Gojko Babić


32-bit ALU

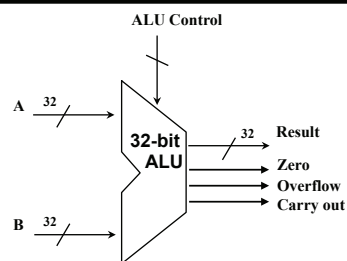

- Our ALU should be able to perform functions:
 - logical **and** function
 - logical **or** function
 - arithmetic **add** function
 - arithmetic **subtract** function
 - arithmetic **slt** (**set-less-then**) function
 - logical **nor** function
- ALU control lines define a function to be performed on A and B.

Functioning of 32-bit ALU

ALU Control lines			
Function	Ainvert	Binvert	Operation
and	0	0	00
or	0	0	01
add	0	0	10
subtract	0	1	10
slt	0	1	11
nor	1	1	00

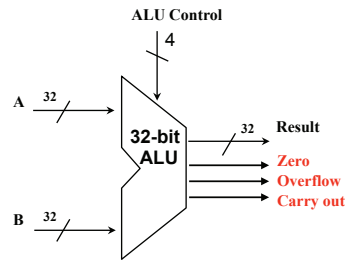

- **Result** lines provide result of the chosen function applied to values of A and B
- Since this ALU operates on 32-bit operands, it is called **32-bit ALU**
- **Zero** output indicates if all Result lines have value 0
- **Overflow** indicates integer overflow of add and subtract functions; for unsigned integers, this overflow indicator does not provide any useful information
- **Carry out** indicates carry out and **unsigned integer overflow**


g. babic

Presentation F

3

Designing 32-bit ALU: Beginning

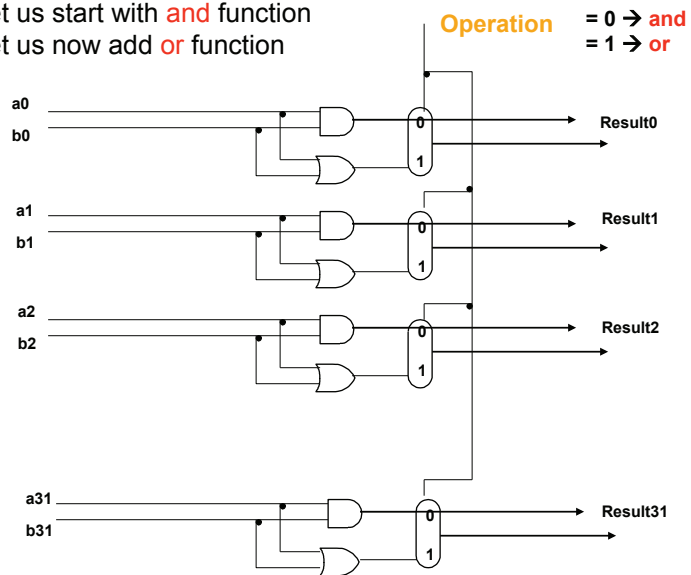1. Let us start with **and** function
2. Let us now add **or** function




g. babic

4

Designing 32-bit ALU: Principles

- A number of functions are performed internally, but only one result is chosen for the output of ALU

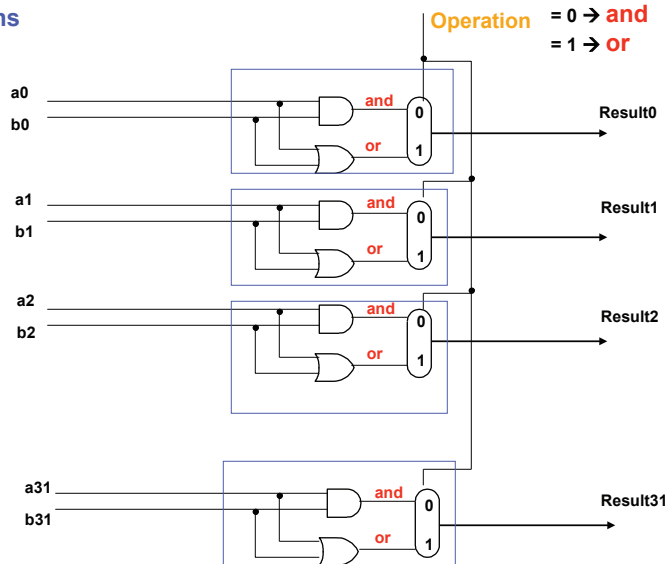- 32-bit ALU is built out of 32 identical 1-bit ALU's




g. babic

5

Designing the Adder

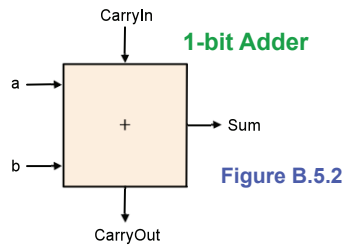- 32-bit adder is built out of 32 1-bit adders



1-bit Adder Truth Table

Input			Output	
a	b	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

From the truth table and after minimization, we can have this design for CarryOut

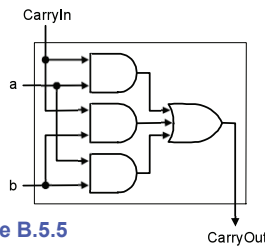


Figure B.5.5


Figure B.5.3

g. babic

Presentation F

6

32-bit Adder

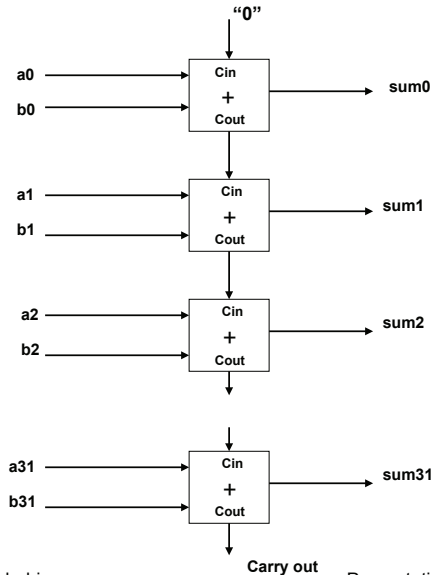

This is a ripple carry adder.


The key to speeding up addition is determining carry out in the higher order bits sooner.
Result: **Carry look-ahead adder.**

g. babic

Presentation F

7

32-bit ALU With 3 Functions

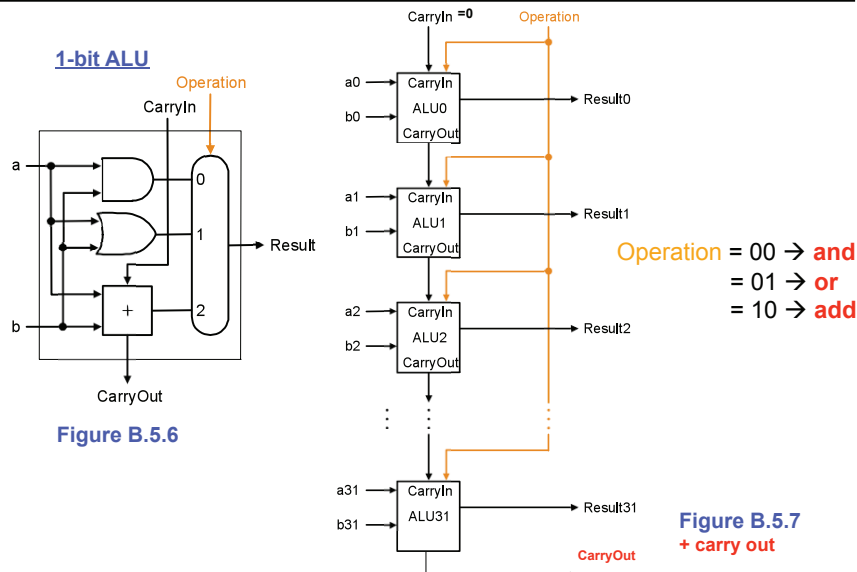

1-bit ALU

Figure B.5.6

Operation = 00 → **and**
 = 01 → **or**
 = 10 → **add**


Figure B.5.7
 + carry out

g. babic

Presentation F

8

32-bit Subtractor

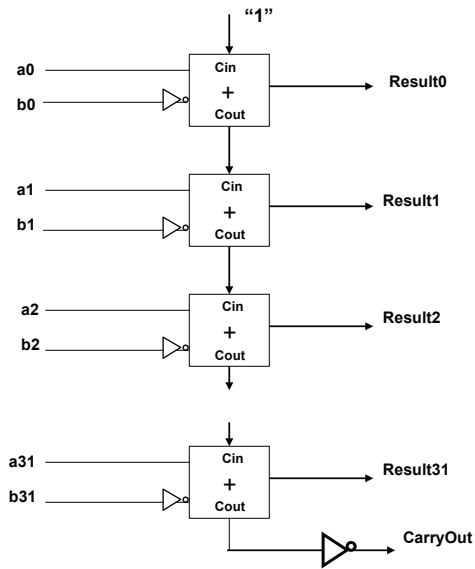

$$A - B = A + (-B)$$


$$= A + \overline{B} + 1$$

g. babic

Presentation F

9

32-bit Adder / Subtractor

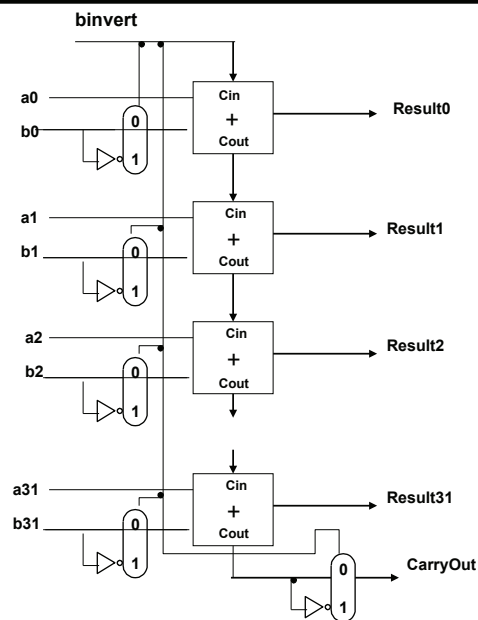


$$\text{Binvert} = 0 \rightarrow \text{addition}$$

$$= 1 \rightarrow \text{subtraction}$$

g. babic


10

32-bit ALU With 4 Functions

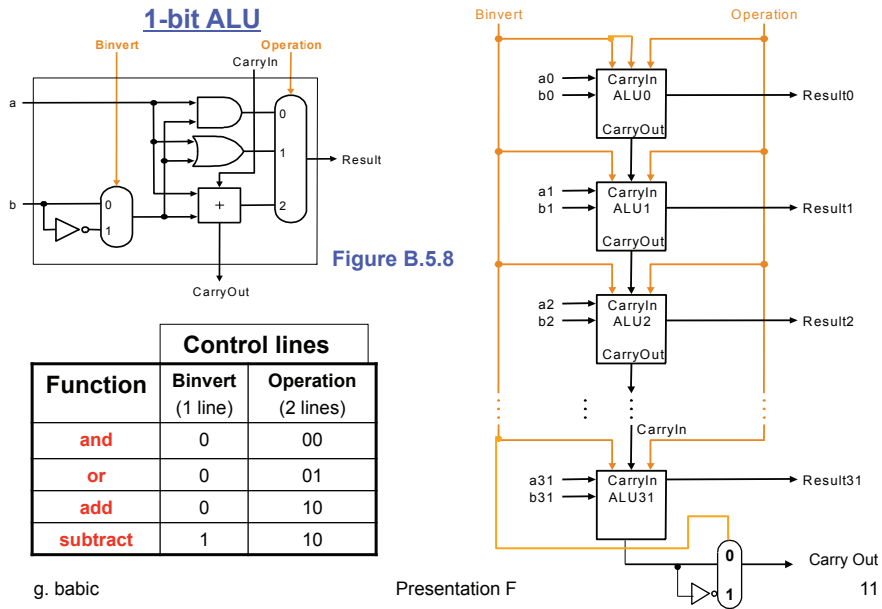

2's Complement Overflow

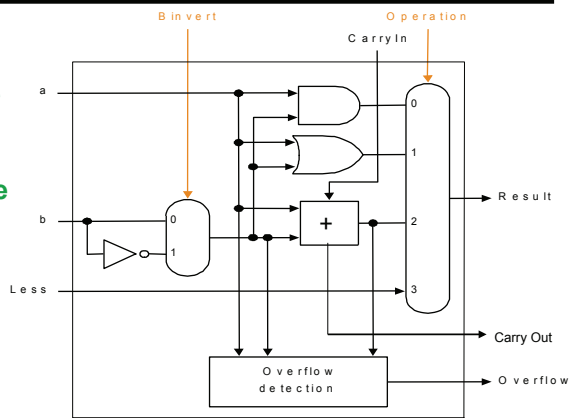- 2's complement overflow happens:
 - if a sum of two positive numbers results in a negative number
 - if a sum of two negative numbers results in a positive number




1-bit ALU for the most significant bit

Other 1-bit ALUs, i.e. non-most significant bit ALUs, are not affected.

32-bit ALU With 4 Functions and Overflow

Function	Control lines	
	Binvert (1 line)	Operation (2 lines)
and	0	00
or	0	01
add	0	10
subtract	1	10

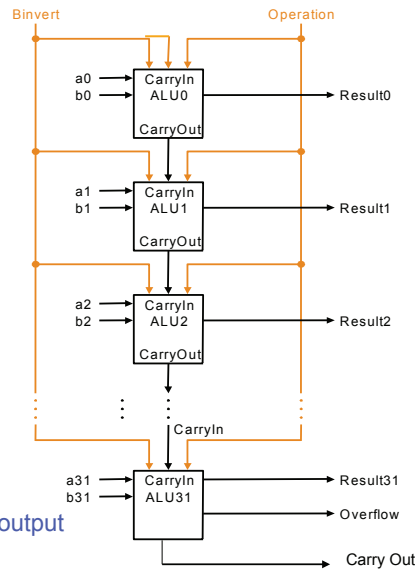

Missing: **slt** & **nor** functions and **Zero** output

g. babic

Presentation F